

- DC-Power Supply HX300/800
  - Arc-Management with resonant circuit
- Unipolar Pulse Generator SD300 / SD301
  - Active Arc-Management
- Bipolar Pulse Generator SB300
  - General Concept
- Arc-Measurement
  - Important Arc Parameters
- Comparison ADL SB300 – Competition

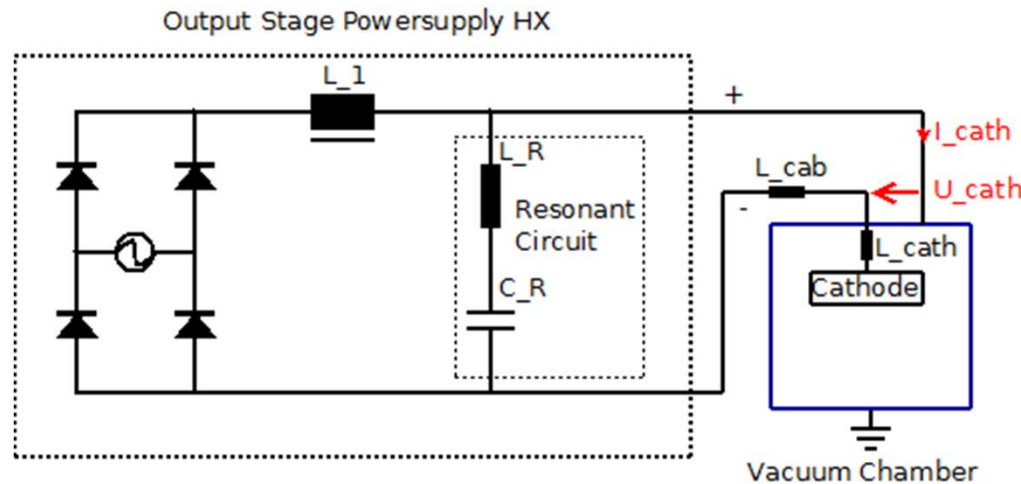


Figure 1: Output Stage

- Inductance  $L_1$  smoothens rectified output current and prevents rapid current increase during arcing
- Inductance  $L_R$  and capacitor  $C_R$  form the resonant circuit
- $L_{cab}$  represents cable inductance
- $L_{cath}$  represents inductance of vacuum chamber

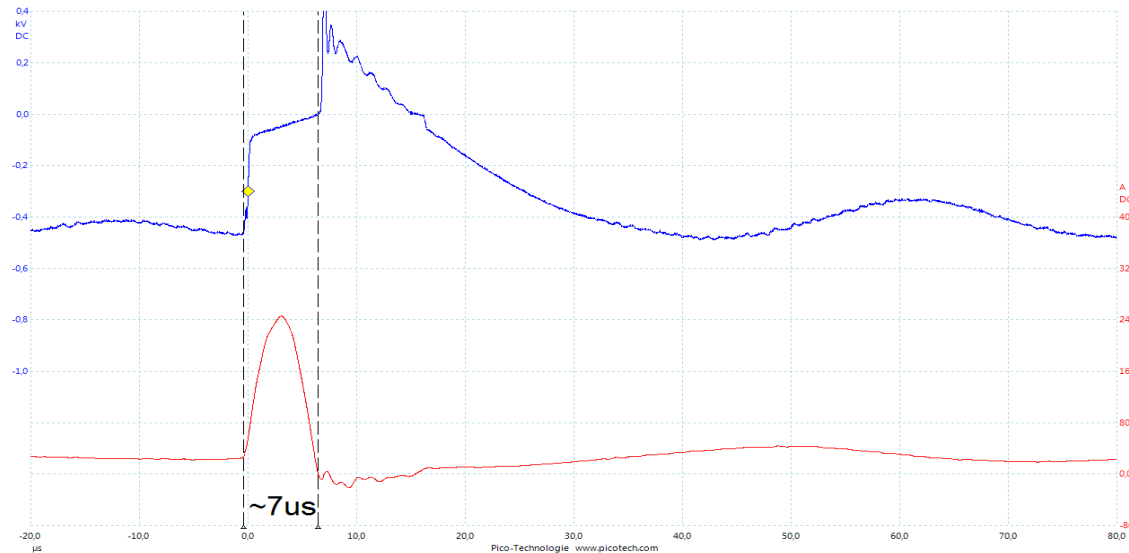


Figure 2: Arc event at HX output

- Voltage - Current

- Arc happens at  $t = 0$ , voltage drops rapidly and current increases
- The arc stimulates the resonant circuit to self-oscillation
- The oscillation leads to a reverse current, quenching the arc at  $t = 7 \mu\text{s}$
- Most arcs can be quenched by resonant circuit
- No power shut down of power supply necessary
- Plasma ignited again after voltage dropped

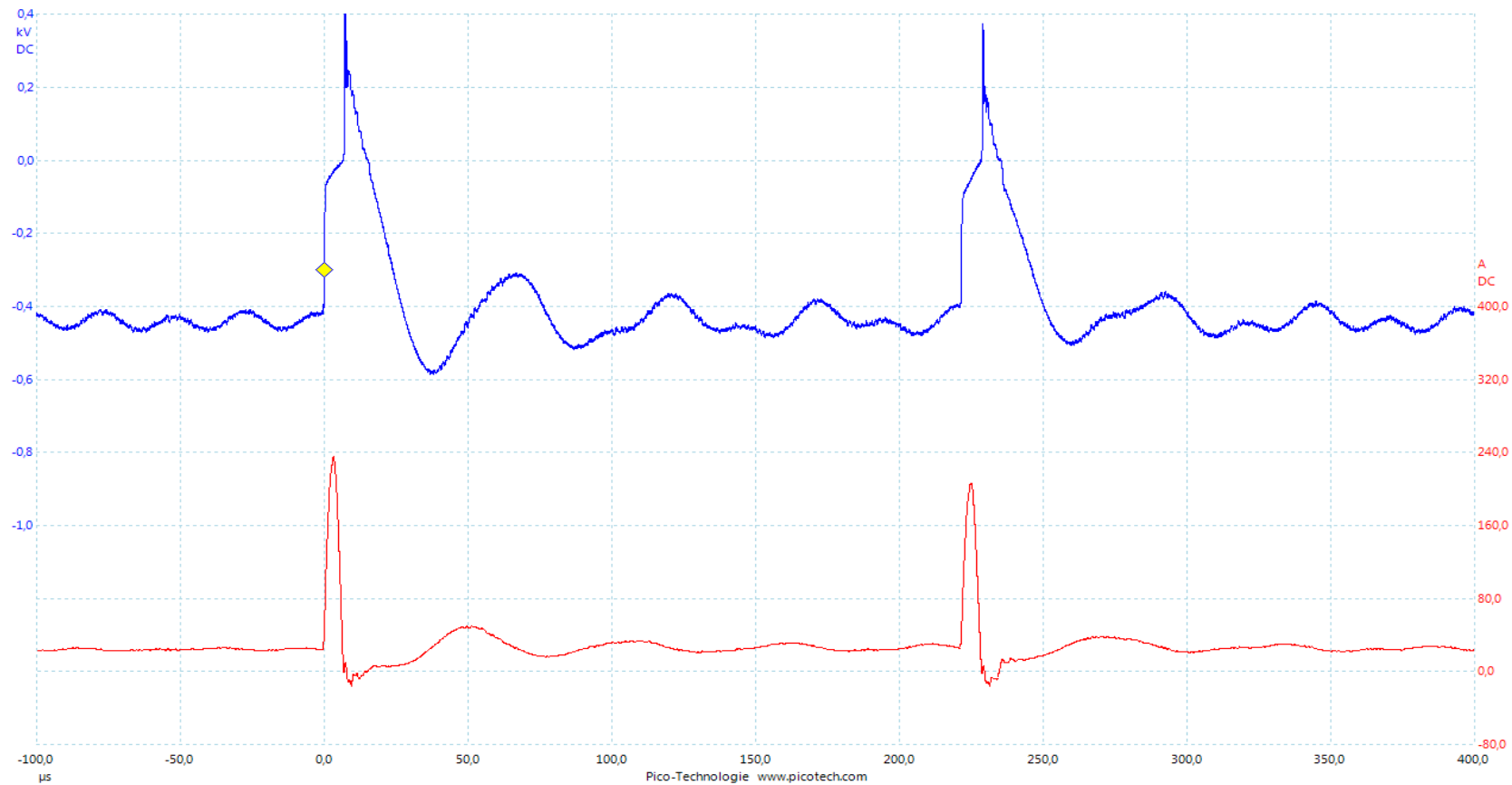


Figure 3: Two arcs in series on larger time scale

- Voltage - Current

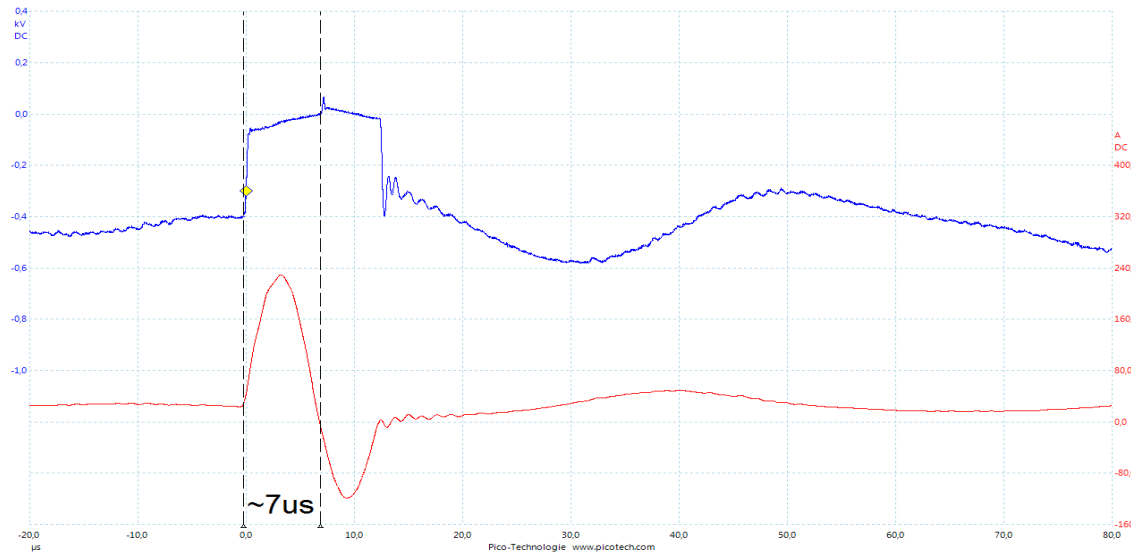


Figure 4: Arc Event with  
Cathode-Clamp Diode  
- Voltage - Current

- Cathode-Clamp diode connected in parallel to the output of HX unit
- Arc happens at  $t = 0$ , voltage drops rapidly and current increases
- No reverse voltage possible, but full reverse current through diode
- Reverse current runs from  $t = 7 \mu\text{s}$  up to  $t = 12 \mu\text{s}$
- Faster ignition of plasma because of no voltage reversal

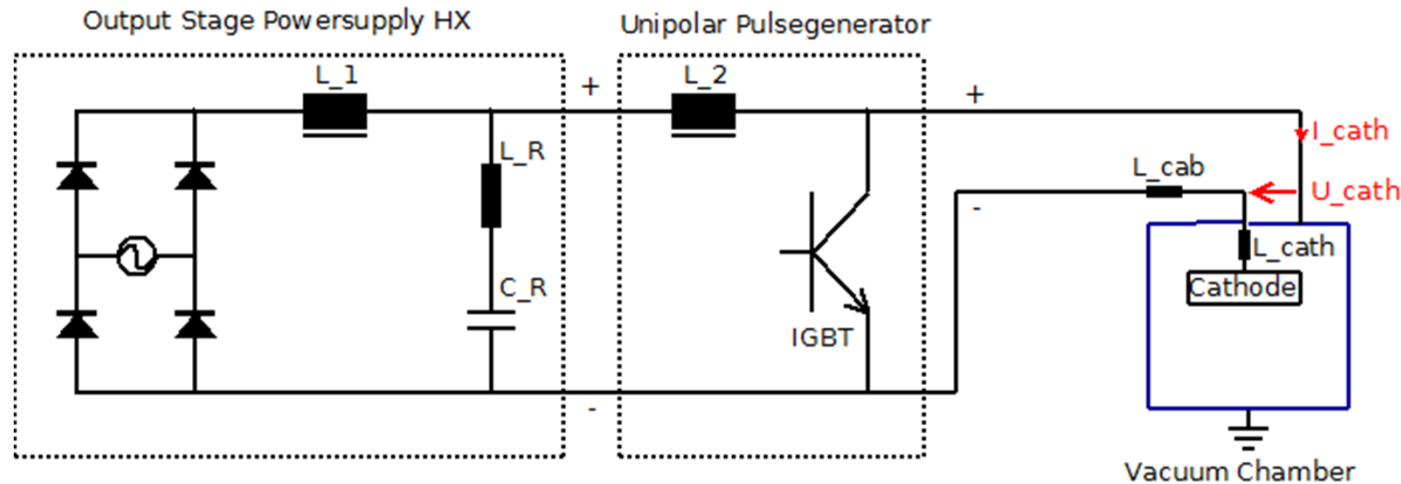


Figure 5: Unipolar Pulse Generator connected between HX and Vacuum Chamber

- Resonant circuit of HX is blocked by large inductance  $L_2$  of pulse generator
- ONLY arc management of pulse generator is active
- Switching IGBT directly at the output of the pulse generator unit
- Current sourcing pulse unit principle
- Active arc handling, switch off with IGBT during arcing

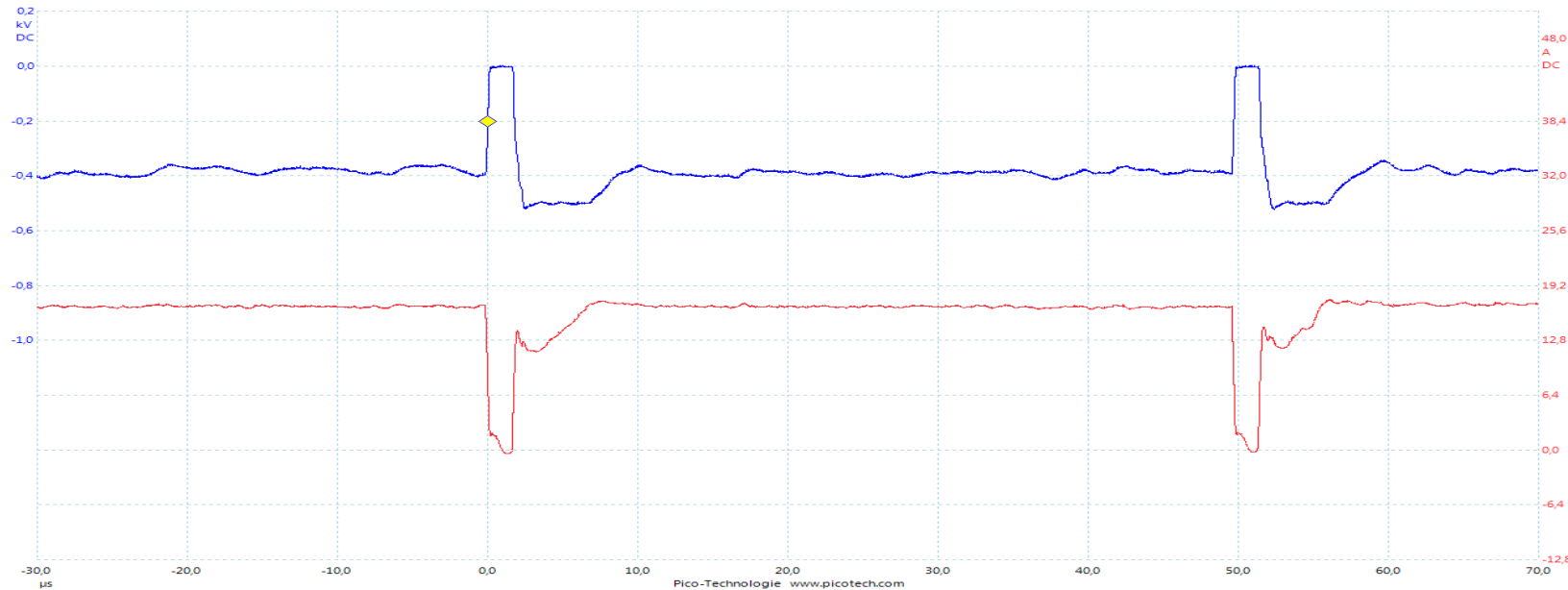


Figure 6: Voltage and Current waveform

- Voltage - Current

- Default setting 20 kHz with 48 µs On-time and 2 µs Off-time
- At  $t = 0$  pulse generator shortens the output for 2 µs Off-time
- After Off-time the IGBT opens again

## HX + Unipolar Pulse Generator SD150/SD300 III



Analoge & Digitale  
Leistungselektronik  
GmbH

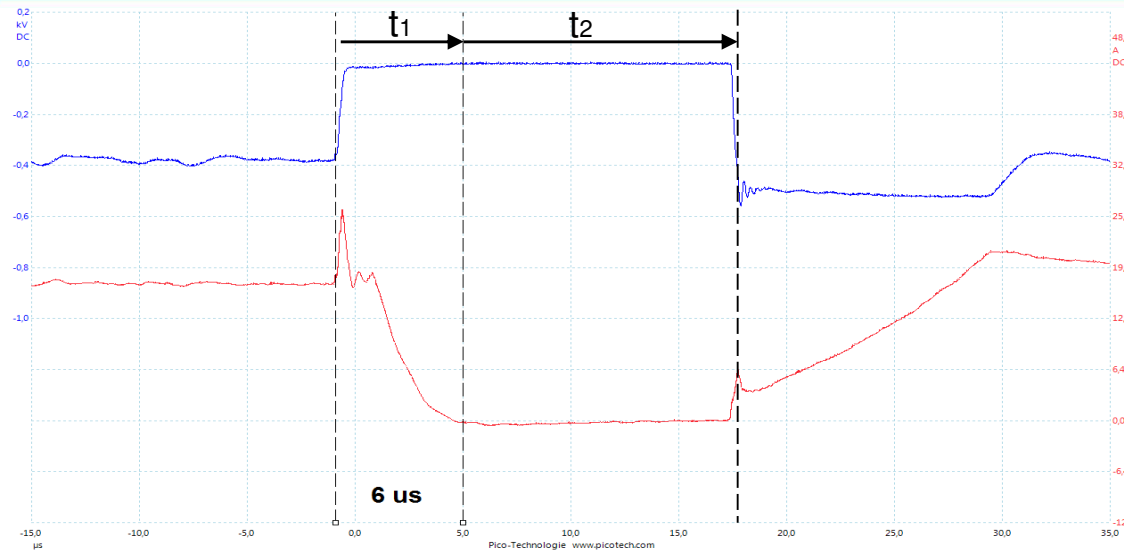


Figure 7: Voltage and Current waveform during arc event

- Voltage - Current

$t_1$  – variable,  
depending on current and  
cable / cathode inductance  
 $t_2$  – Pause time variable,  
automatically adjusted

- At  $t = 0$  an arc event occurs
- The cathode current increases rapidly
- Maximum 1.5  $\mu\text{s}$  after arc occurs the pulse generator shuts down
- Cathode current decreases and arc is quenched after 6  $\mu\text{s}$  in this case
- The pulse generator restarts after additional 13  $\mu\text{s}$  in this specific case



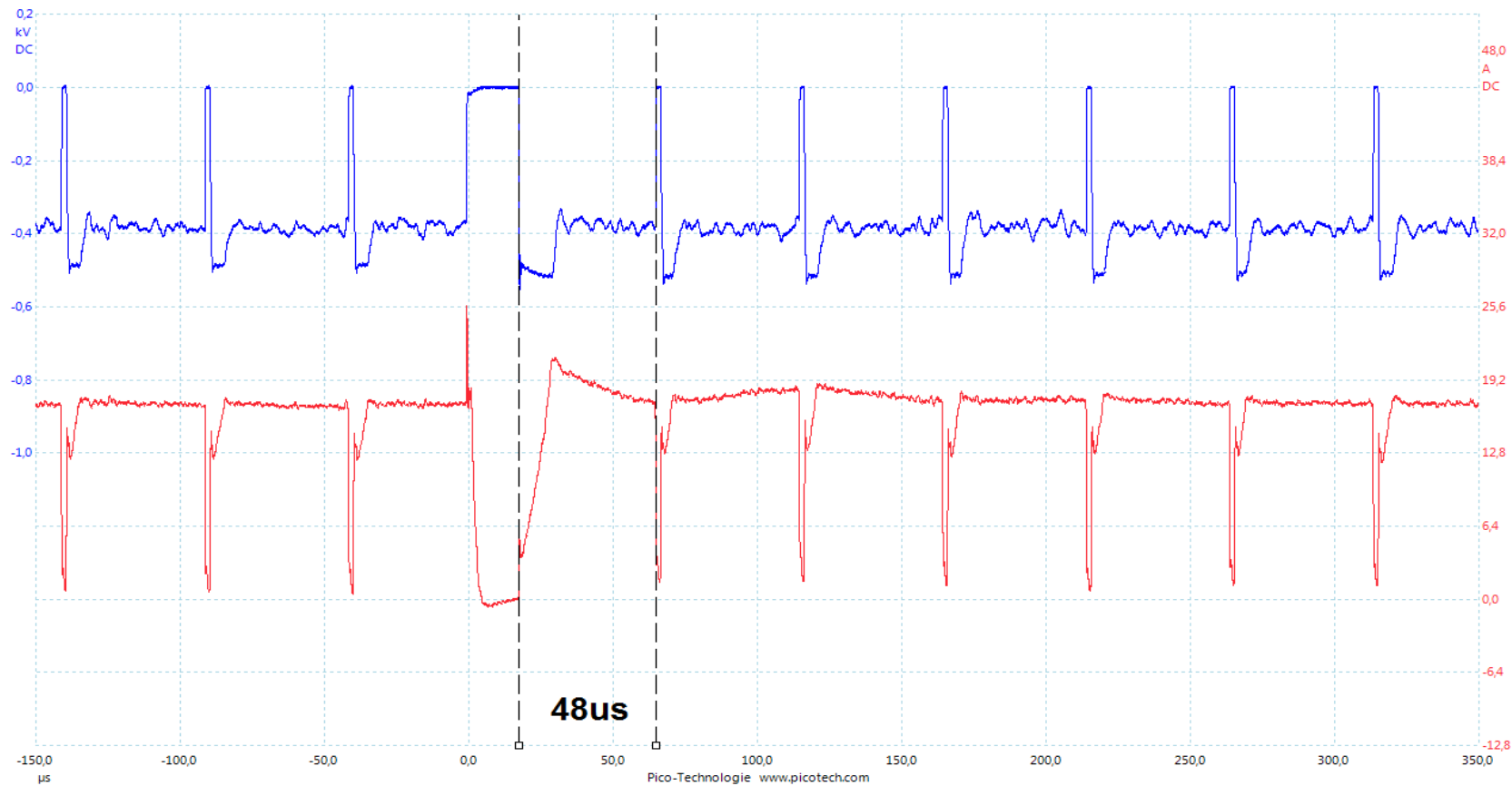


Figure 8: Arc event at end of pulse period on larger time scale

- Voltage - Current

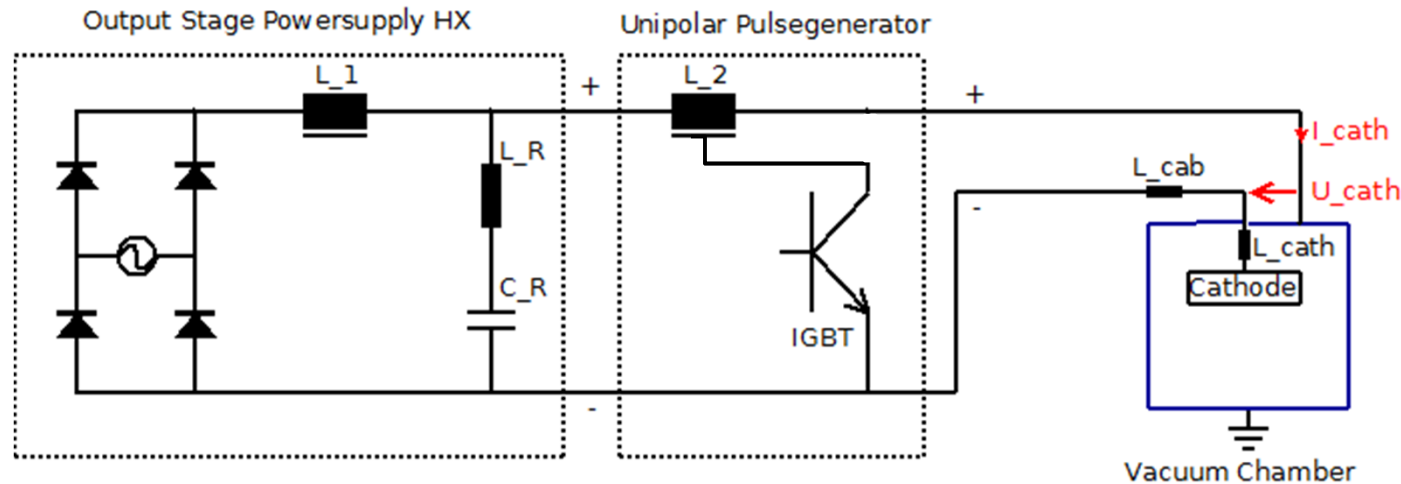


Figure 9: Unipolar Pulse Generator connected between HX and Vacuum Chamber

- Resonant circuit of HX is blocked by large inductance  $L_2$  of pulse generator
- ONLY arc management of pulse generator is active
- Switching IGBT at tap of  $L_2$
- Current sourcing pulse unit principle
- Active arc handling, switch off with IGBT during arcing

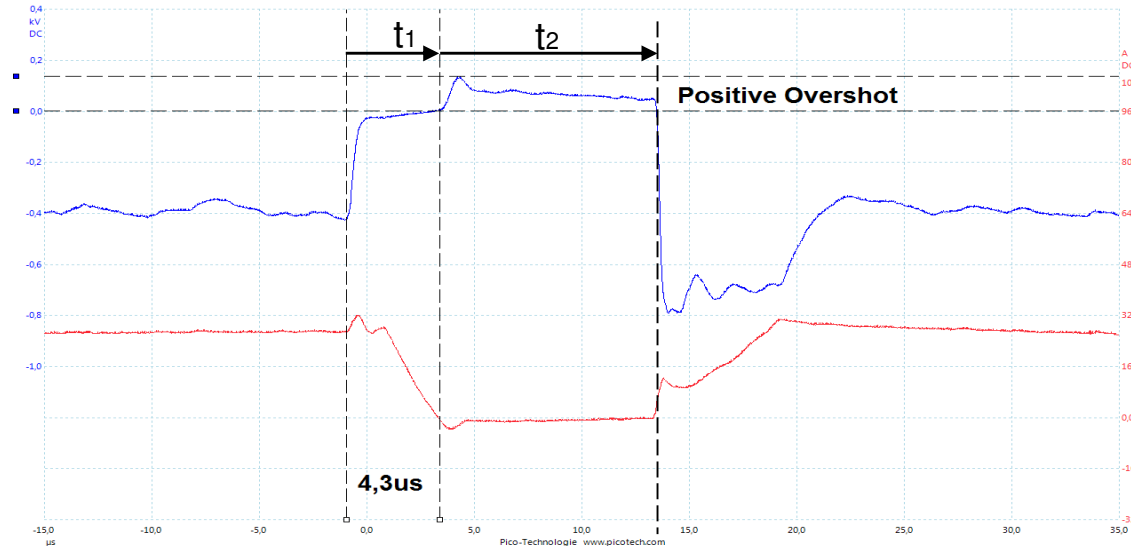


Figure 10: Voltage and Current waveform during arc event with reverse pulse

- Voltage - Current

$t_1$  – variable,  
depending on current and  
cable / cathode inductance  
 $t_2$  – Pause time variable,  
automatically adjusted

- At  $t = 0$  an arc event occurs
- The cathode current increases rapidly
- Maximum 1.5  $\mu\text{s}$  after arc occurs the generator shuts down
- Cathode current decreases and arc is quenched after 4.3  $\mu\text{s}$  in this case
- The pulse generator restarts after additional 10  $\mu\text{s}$  in this specific case
- Faster arc quenching and lower arc energy compared to SD150/300

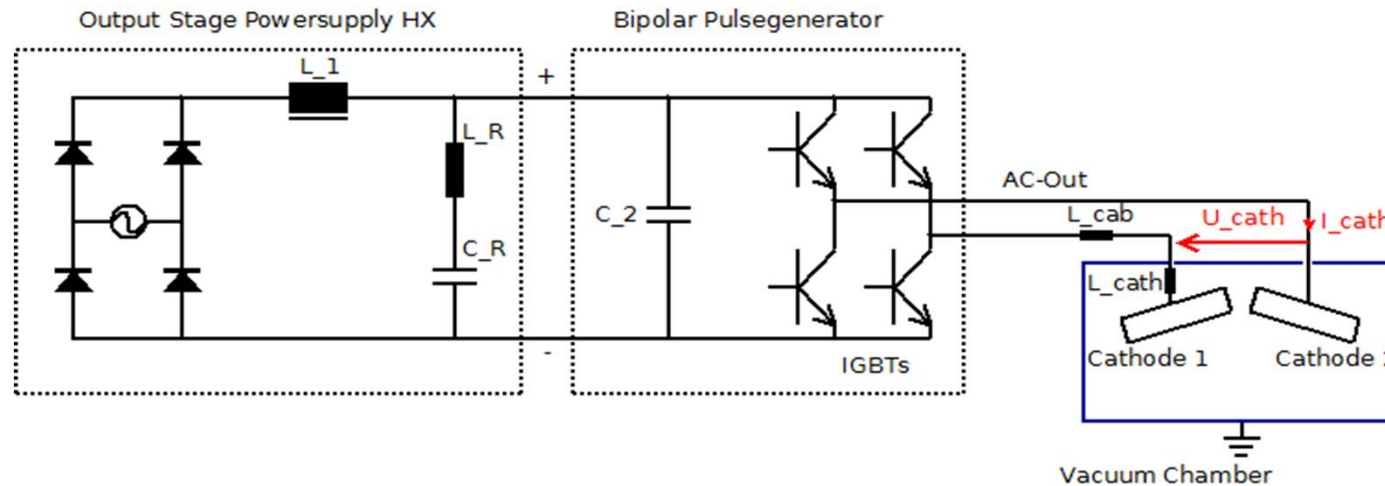


Figure 11: Bipolar Pulse Generator connected between HX and Vacuum Chamber

- ONLY arc management of pulse generator is active
- Capacitor  $C_2$  holds voltage constant over half waves
- Switching H-bridge of IGBT and clamp diodes directly at the output of the pulse generator unit
- Voltage sourcing pulse unit principle

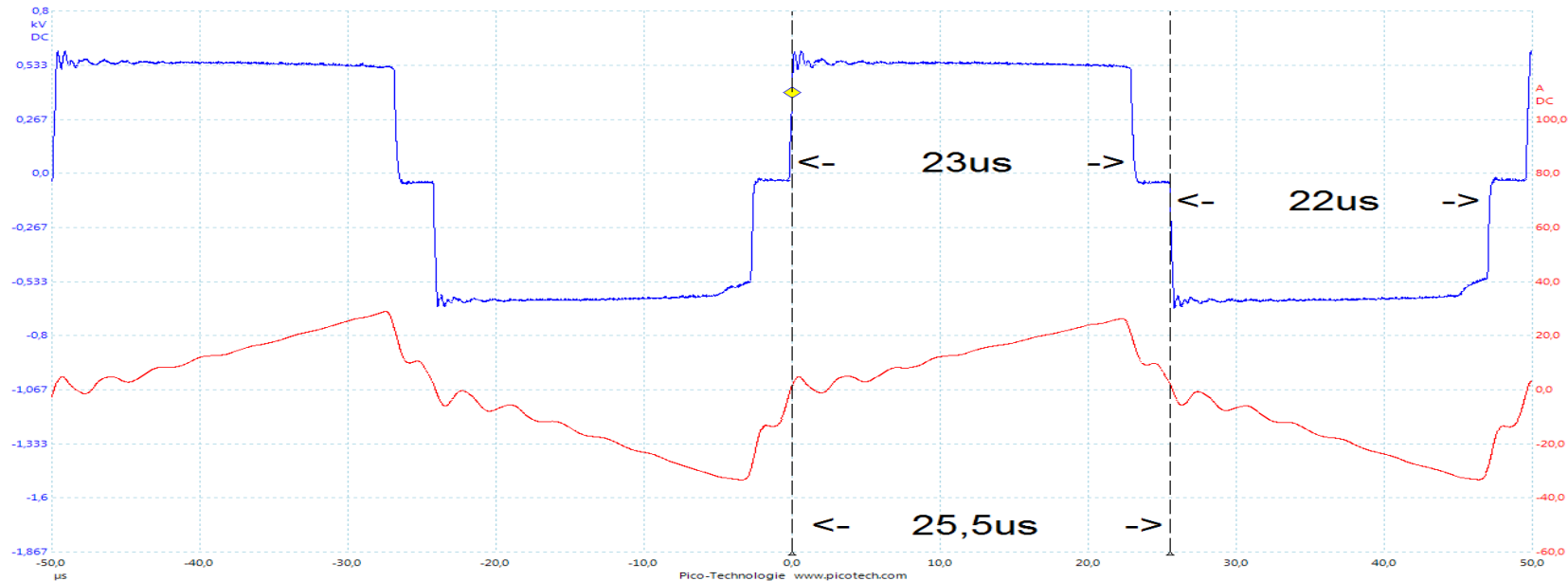


Figure 12: Voltage and Current waveform of SB300

- Voltage - Current

- Fixed setting of 20 kHz pulse frequency, unsymmetrical operation possible
- Fixed pause-time of 2.5 μs between positive and negative half wave
- Voltage constant and current ramps up during half wave

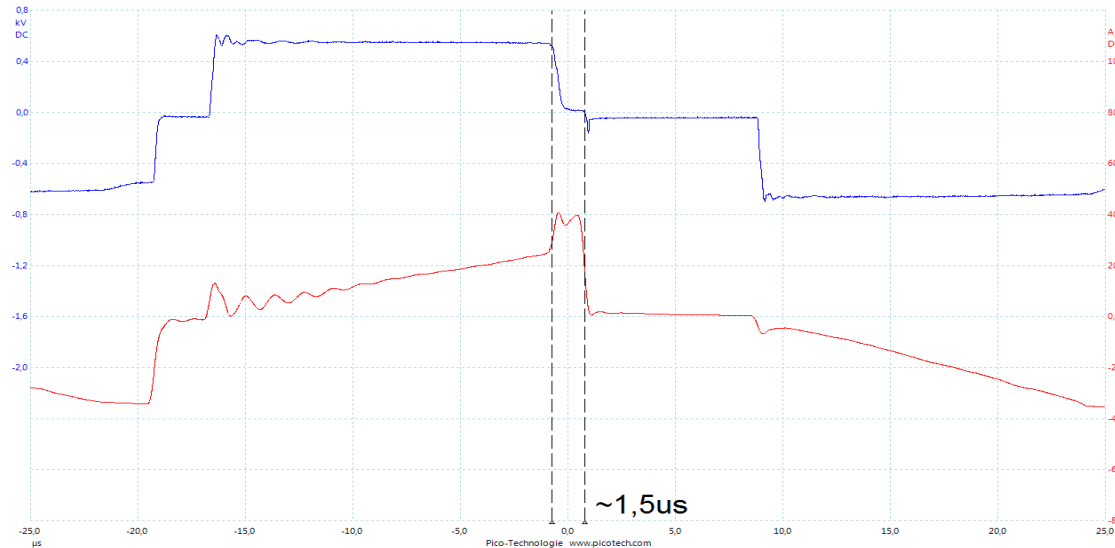


Figure 13: Voltage and Current waveform during arc event

- Voltage - Current

- At the end of the positive half wave an arc event occurs
- The cathode current increases rapidly and voltage collapses
- 1.5  $\mu$ s after the arc occurs, it gets quenched
- For the remaining time of the half wave there will be paused
- The SB300 pulse generator restarts with the next half wave

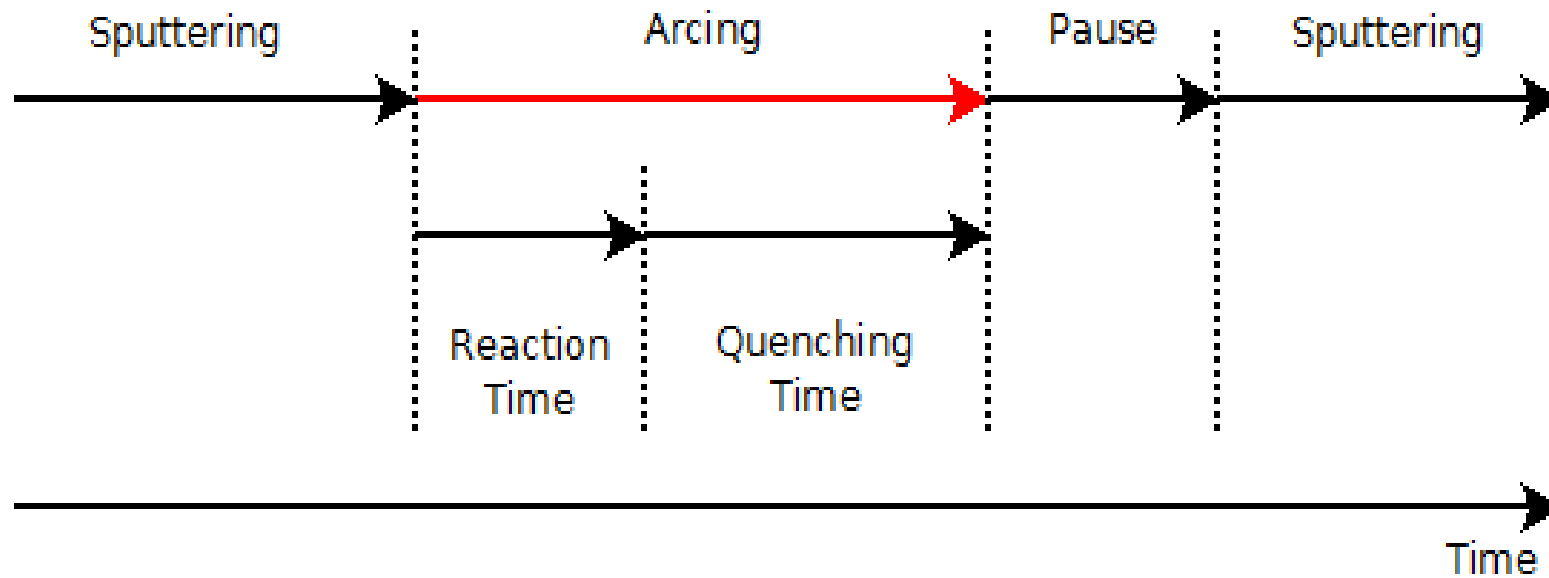


Figure 14: Different time periods during arc events

# Overview of arc-measurements



Analoge & Digitale  
Leistungselektronik  
GmbH

	DC Power-Supply (HX 300/800)	Pulsed DC (HX 300/800 + SD 300)	Bipolar Pulse (HX 300/800 + SB 300)
Measurement Conditions - Regulation-Mode of DC-Unit - Output Power of DC-Unit - Output Voltage of DC-Unit - Output Inductance $L_{out}$	Power 10 kW ~ 450 V ~ 2 $\mu$ H	Power 10 kW ~ 450 V ~ 2 $\mu$ H	Power 10 kW ~ 560 V ~ 2 $\mu$ H
Reaction Time	0 $\mu$ s	< 1,5 $\mu$ s	< 1 $\mu$ s
Quenching time	7 $\mu$ s	~ 5 $\mu$ s (variable)	~ 0.5 – 1.5 $\mu$ s
Pause	0 $\mu$ s (no shut down)	~ 12.5 $\mu$ s (variable)	0 – 22.5 $\mu$ s
Process to eliminate the arc	Reverse current achieved by resonant circuit	Short circuit the cathode current until it is almost zero, then a pause.	Open circuit, start with new pulse.
Arc energy	~ 2.5 mJ/kW	~ 0.25 mJ/kW	~ 0.15 mJ/kW
Maximal output inductance	Max. 10 $\mu$ H for cable + cathode	Max. 10 $\mu$ H for cable + cathode	Max. 10 $\mu$ H for cable + cathode
Maximal arc-handling per second	~ 40.000 without clamp diode ~ 75.000 with clamp diode	50.000	40.000



## Sinewave - Pulse: comparing different technologies

	Sine-Wave	Actual competitors Bip-Power Supplies	Bipolar ADL Bip-Power Supplies
Ignition Voltage	1600 -2000V	1600 -2000V	500-1000V
Wave form voltage	Sine (distorted)	Trapeze descending after voltage peak	rectangle
Wave form current	Sine	Rectangle (distorted)	Trapeze ascending
Highest Arc-probability	Mid of Half-Wave 90° and 270°	Start of Half-Wave 0° and 180°	End of Half-Wave 180° and 360°
Arc-Energy	big	low	low
Voltage-Difference Cathode 1/2	medium	big	low
Power-Difference Cathode 1/2	low (Balanced with AC-coupling)	big (Simple control)	very low (Power ratio controller)
Over-Voltage Stress	low (Sine)	big (Voltage peaks)	no (Square wave)
Dimensions	big	medium	small

A large blue rectangular area with a white geometric shape on the left side. The white shape consists of a horizontal line at the top, a diagonal line sloping down to the left, and a horizontal line at the bottom. The text 'Thank You For Your Attention' is written in white, sans-serif font, centered within the blue area.

Thank You For Your  
Attention